

AC CIRCUITS & TIME VARYING SIGNALS

01205479 IoT for EE

Dr.Varodom Toochinda

Dept. of Mechanical Engineering, Kasetsart University

- ▶ Capacitors
- ▶ Inductors
- ▶ Periodic Signals
- ▶ Phasor Method
- ▶ System concepts
- ▶ LPF and other noise filtering techniques


OUTLINE

CAPACITORS


capacitance

$$C = \frac{\epsilon A}{d}$$


Farad

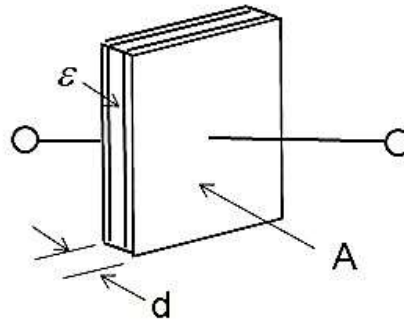

Physical structure

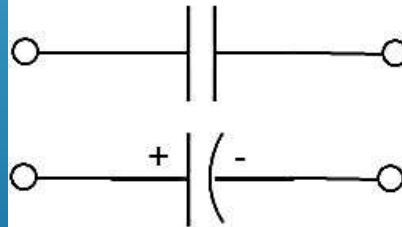

Symbol

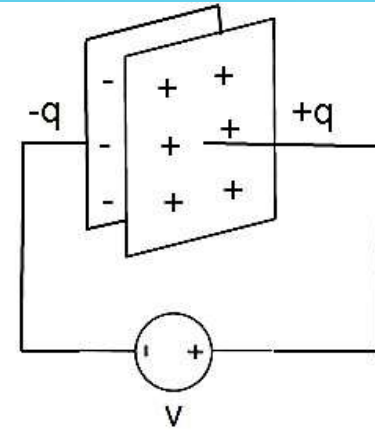

Capacitor when voltage is applied




Different types of capacitors

VOLTAGE AND CURRENT


Charge : $q(t) = Cv_c(t)$

Current : $i_c(t) = \frac{dq(t)}{dt} = C \frac{dv_c(t)}{dt}$

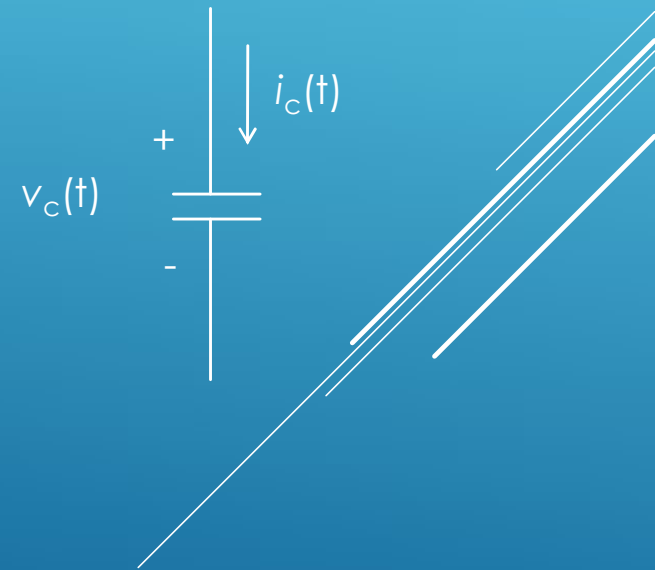Voltage : $v_c(t) = \frac{1}{C} \int_{-\infty}^t i_c(\tau) d\tau$




TOTAL CAPACITANCE

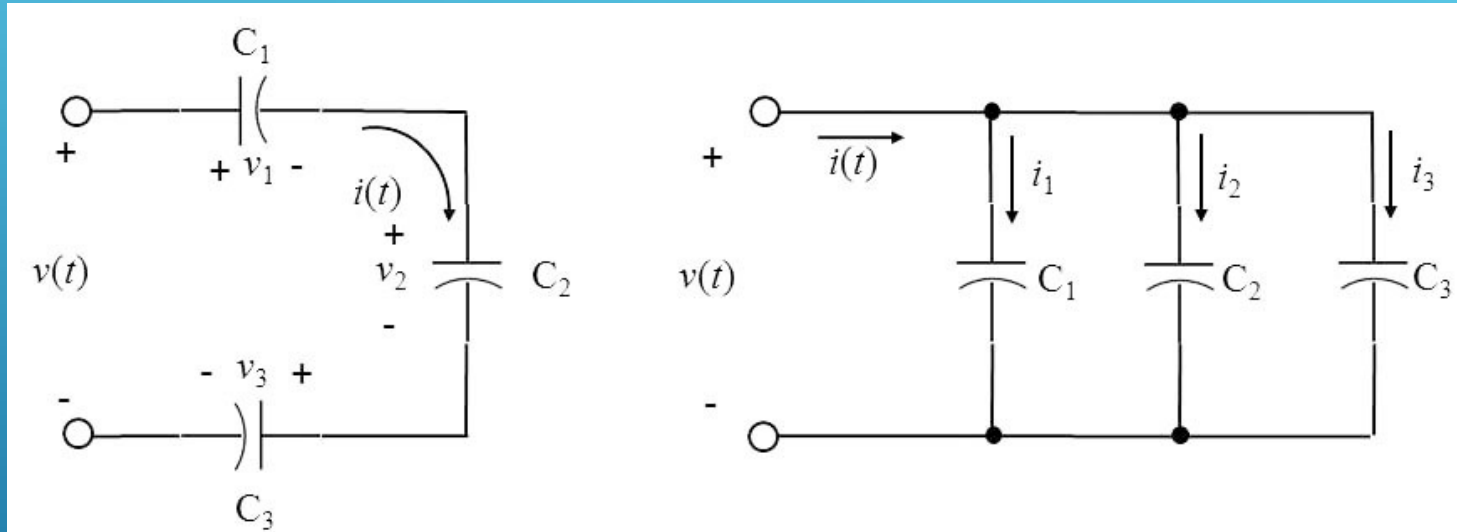


$$C_{eq} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}}$$

$$C_{eq} = C_1 + C_2 + C_3$$


INDUCTORS

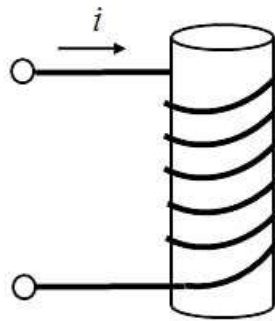

Physical structure

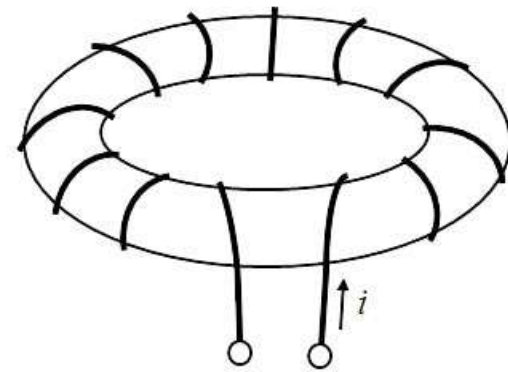

Toroid type

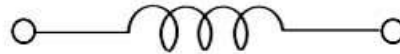

Symbol



Different types of inductors

VOLTAGE AND CURRENT


Current

$$i_L(t) = \frac{1}{L} \int_{-\infty}^t v_L(\tau) d\tau$$

Voltage

$$v_L(t) = L \frac{di_L(t)}{dt}$$


TOTAL INDUCTANCE

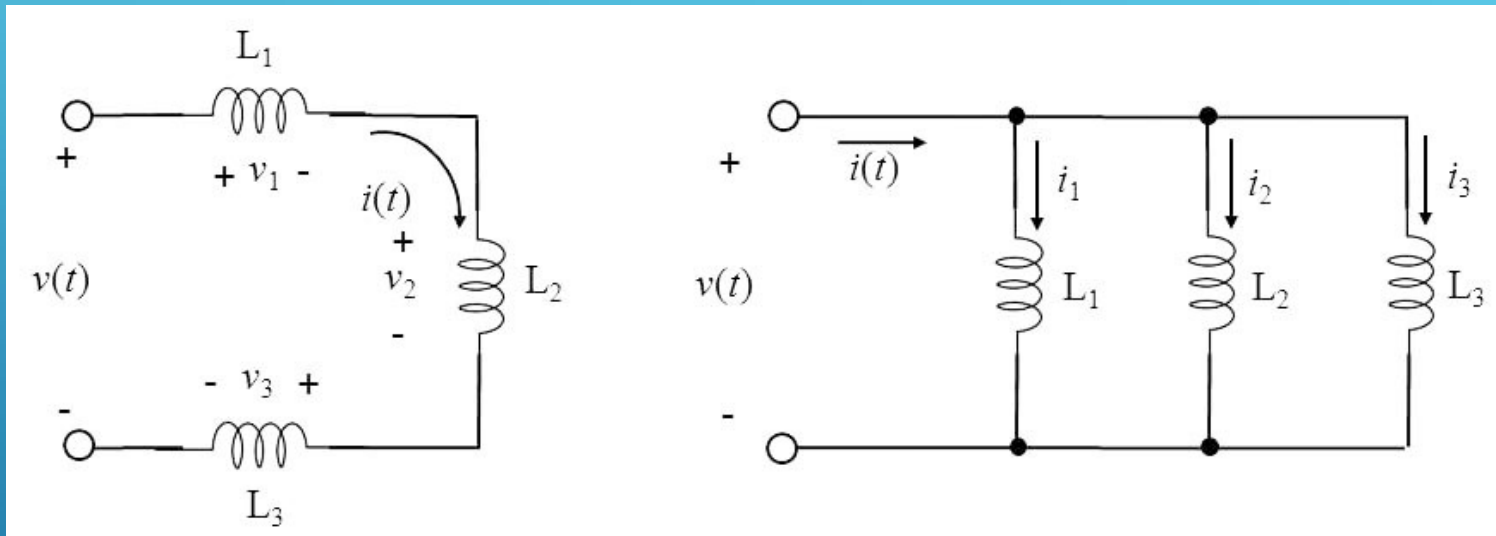


$$L_{eq} = L_1 + L_2 + L_3$$

$$L_{eq} = \frac{1}{\frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3}}$$


PERIODIC SIGNALS

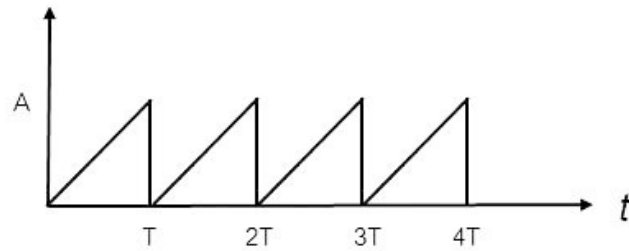


Sawtooth

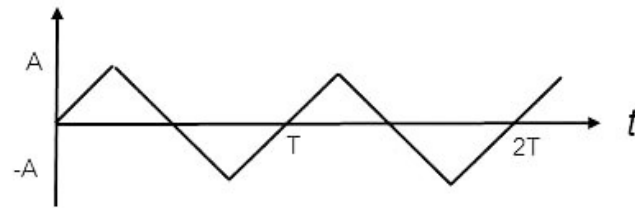


Triangle

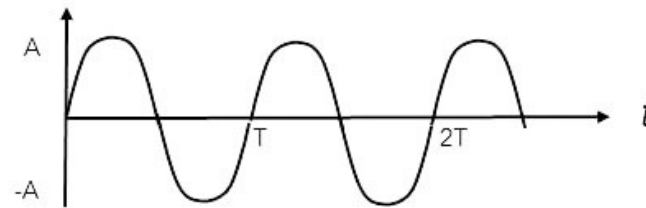


Sine

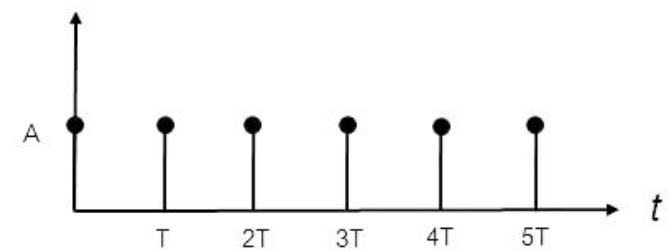

Impulse

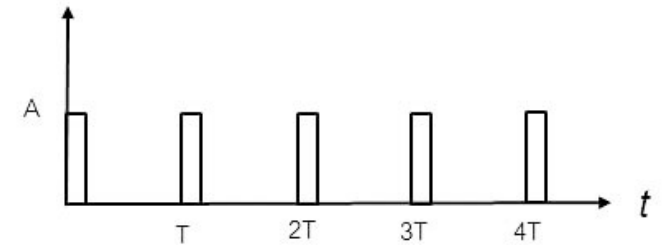

Pulse

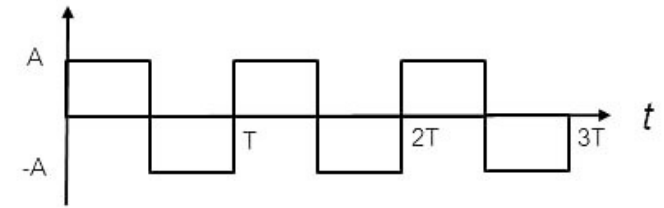

Square

SINUSOID

$$x(t) = A \cos(\omega t + \phi)$$

↑
magnitude

↑
frequency: radian

↑
phase

$$A \sin(\omega t) = A \cos\left(\omega t - \frac{\pi}{2}\right)$$


Exercise: write Python code to plot sine and cosine waveforms

PHASOR METHOD

sinusoid signal $v(t) = A \cos(\omega t + \theta)$

phasor $V(j\omega) = Ae^{j\theta} = A \angle \theta$

frequency dependent magintude phase





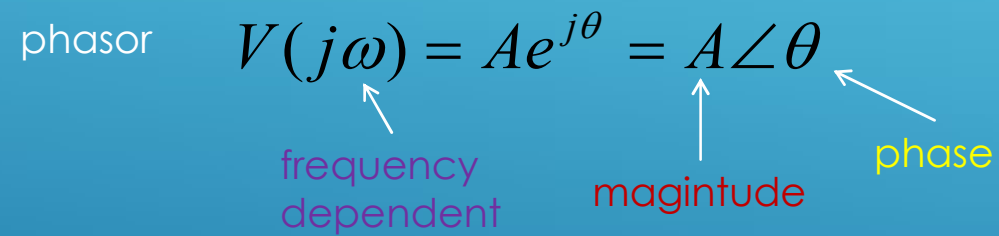


Applicable when all signals in a circuit have only one common frequency

IMPEDANCE

$$v_S(t) = A \cos \omega t$$
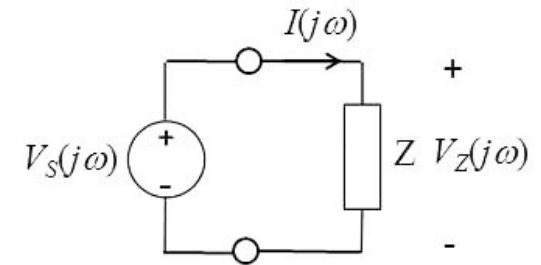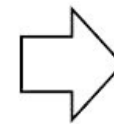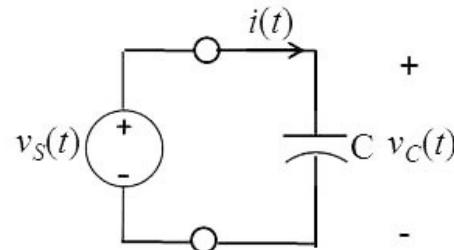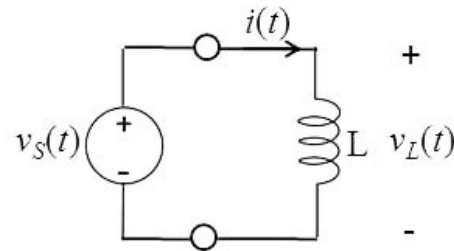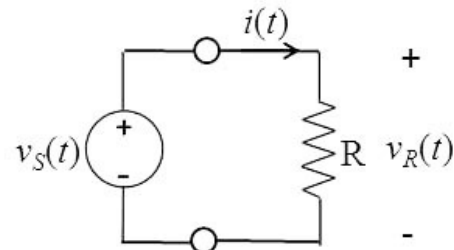
$$V_S(j\omega) = Ae^{j\theta} = A\angle\theta$$



RESISTORS


$$v = iR$$

$$i(t) = \frac{v_s(t)}{R} = \frac{A}{R} \cos \omega t$$

$$V_s(j\omega) = A \angle 0$$

$$I(j\omega) = \frac{A}{R} \angle 0$$
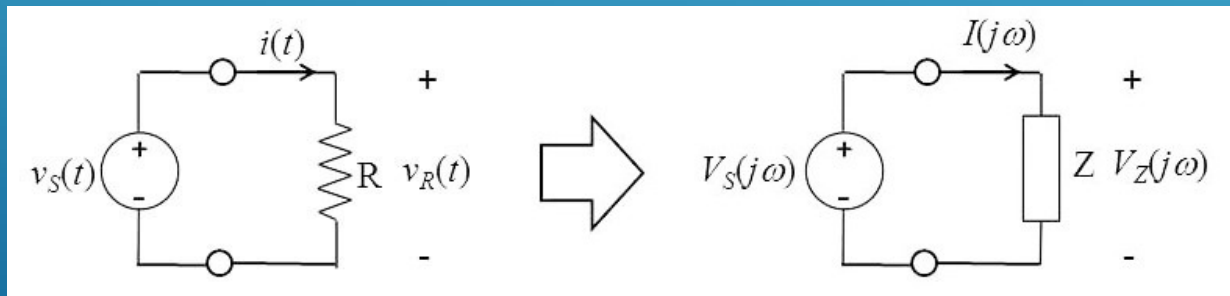
$$Z_R(j\omega) = \frac{V_s(j\omega)}{I(j\omega)} = R$$



INDUCTORS


$$\begin{aligned}i(t) &= \frac{1}{L} \int v_s(\tau) d\tau \\&= \frac{1}{L} \int A \cos \omega \tau d\tau \\&= \frac{A}{\omega L} \sin \omega t\end{aligned}$$

$$i(t) = \frac{A}{\omega L} \cos\left(\omega t - \frac{\pi}{2}\right)$$

$$V_s(j\omega) = A \angle 0$$

$$I(j\omega) = \frac{A}{\omega L} \angle -\frac{\pi}{2}$$
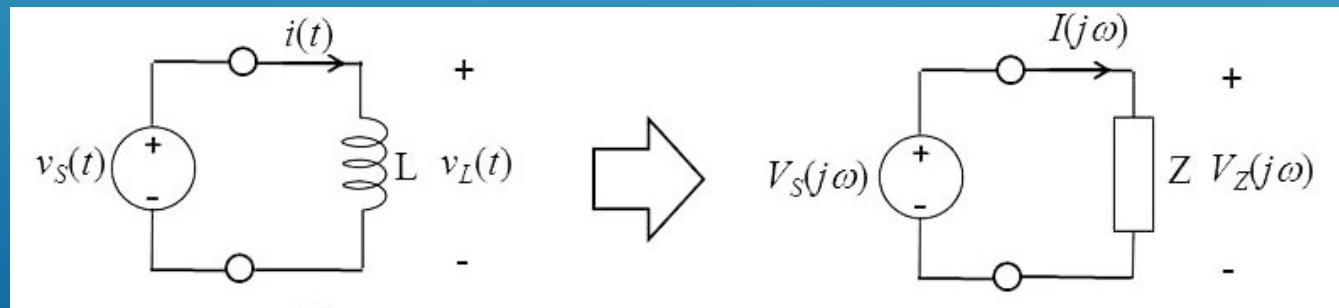
$$Z_L(j\omega) = \frac{V_s(j\omega)}{I(j\omega)} = \omega L \angle \frac{\pi}{2} = j\omega L$$



CAPACITORS


$$\begin{aligned} i(t) &= C \frac{dv_s(t)}{dt} \\ &= C \frac{d}{dt}(A \cos \omega t) \\ &= -C(A\omega \sin \omega t) \end{aligned}$$

$$i(t) = \omega C A \cos\left(\omega t + \frac{\pi}{2}\right)$$

$$V_s(j\omega) = A \angle 0$$


$$I(j\omega) = \omega C A \angle \frac{\pi}{2}$$
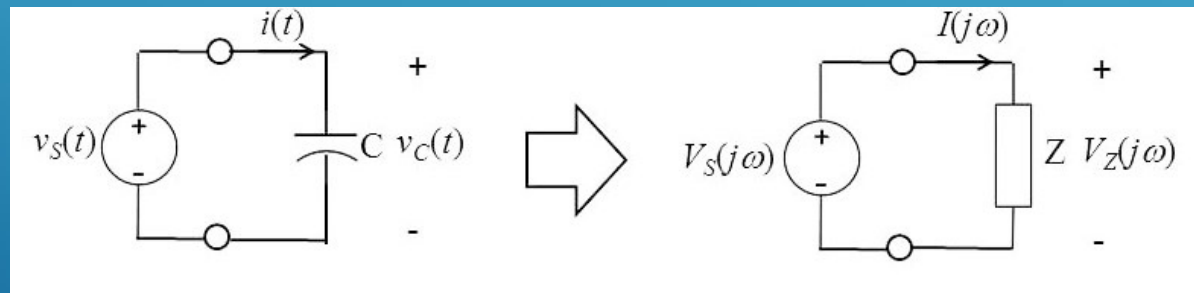
$$\begin{aligned} Z_c(j\omega) &= \frac{V_s(j\omega)}{I(j\omega)} = \frac{1}{\omega C} \angle -\frac{\pi}{2} \\ &= \frac{-j}{\omega C} = \frac{1}{j\omega C} \end{aligned}$$



IMPEDANCE OF RLC CIRCUIT
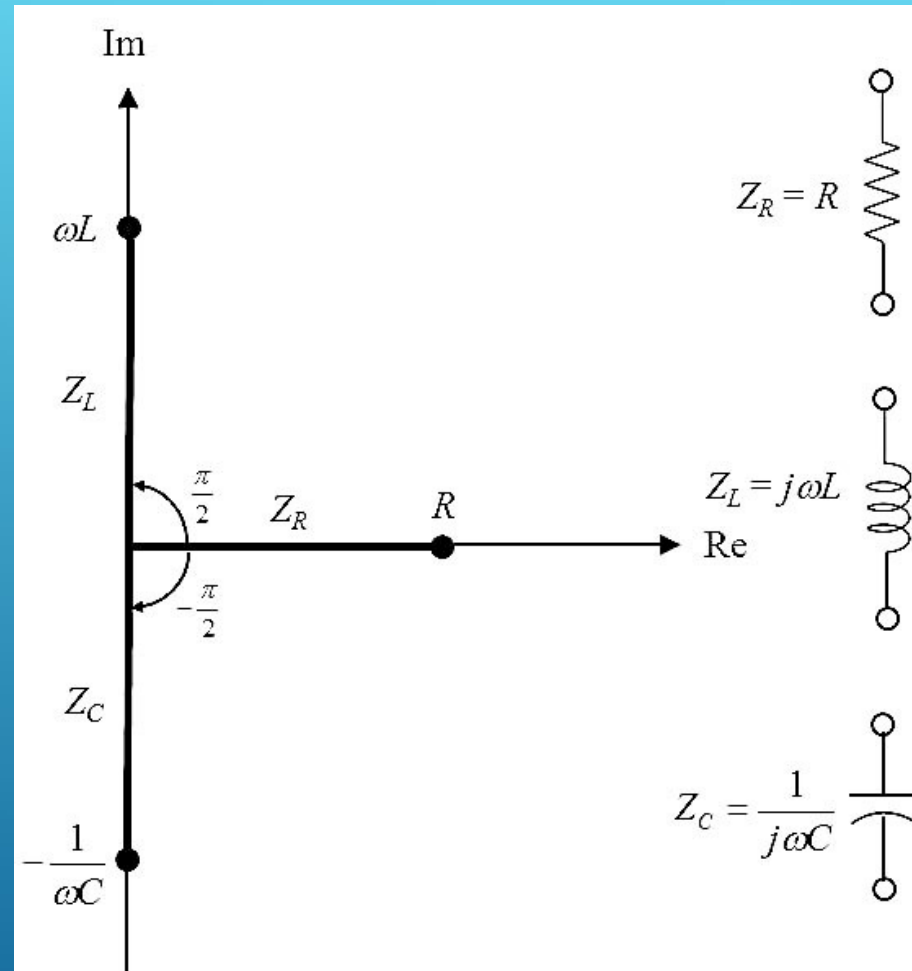
$$Z(j\omega) = R(j\omega) + jX(j\omega)$$



TOTAL IMPEDANCE

Series :

$$Z_{EQ} = \sum_{n=1}^N Z_n$$

Parallel :

$$Z_{EQ} = \frac{1}{1/Z_1 + 1/Z_2 + \dots + 1/Z_N}$$

VOLTAGE/CURRENT DIVIDER

Voltage divider

$$V_n = \frac{Z_n}{Z_1 + Z_2 + \dots + Z_n + \dots + Z_N} V_S$$

Current divider


$$I_n = \frac{1/Z_n}{1/Z_1 + 1/Z_2 + \dots + 1/Z_n + \dots + 1/Z_N} I_S$$

A 3D network diagram is shown on a dark blue background. It consists of ten nodes, which are grey cylindrical rings of varying sizes, connected by thin, light blue lines. The nodes are arranged in a non-uniform pattern, with some having multiple connections. The lighting creates soft shadows on the surface.

SYSTEM CONCEPTS

Frequency responses & transfer functions

FREQUENCY RESPONSE OF AC CIRCUITS

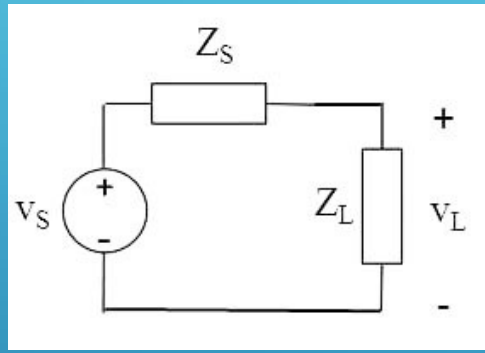

$$V_L = \frac{Z_L}{Z_S + Z_L} V_S$$
$$\frac{V_L}{V_S} = \frac{Z_L}{Z_S + Z_L}$$

$$V_L(j\omega) = H(j\omega)V_S(j\omega)$$

$$V_L e^{j\phi_L} = |H| e^{j\angle H} V_S e^{j\phi_S} = |H| V_S e^{j\angle H + \phi_S}$$

$$V_L = |H| V_S$$


magnitude

$$\phi_L = \angle H + \phi_S$$

phase


LINEAR TIME INVARIANT (LTI) SYSTEMS

transfer function

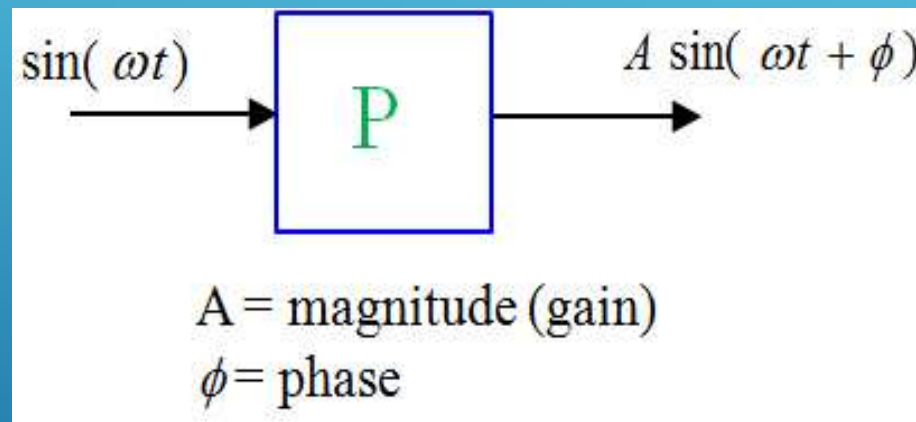

Math tool : Laplace Transform

EXAMPLE: RLC CIRCUIT

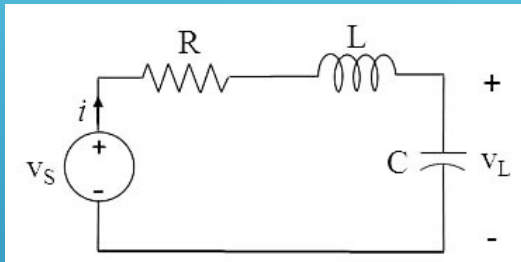

Let $R = 100 \, \Omega$, $C = 10 \, \mu\text{F}$ and $L = 5 \, \text{mH}$

KVL: $\Rightarrow iR + L \frac{di}{dt} + v_L = v_S$

$$i = C \frac{dv_L}{dt} \Rightarrow RC \frac{dv_L}{dt} + LC \frac{d^2 v_L}{dt^2} + v_L = v_S$$

Laplace's $\Rightarrow RCs v_L(s) + LCs^2 v_L(s) + v_L(s) = v_S(s)$

Substitution \Rightarrow

$$P(s) = \frac{v_L(s)}{v_S(s)} = \frac{1}{LCs^2 + RCs + 1} \Rightarrow \boxed{P(s) = \frac{1}{0.05s^2 + 0.001s + 1}}$$

EXERCISE:

Create transfer function using Python control library and plot frequency response

$$P(s) = \frac{1}{0.05s^2 + 0.001s + 1}$$

Useful commands:

```
import control as ctl  
s = ctl.tf('s')  
  
_,_,_ = ctl.bode_plot(P,dB=True,omega_limits=(0.01,1000))
```

Relationships between transfer function and frequency response




$$P(j\omega) = P(s) \Big|_{s=j\omega}$$

$$P(s) = \frac{1}{0.05s^2 + 0.001s + 1}$$




$$\begin{aligned} P(j\omega) &= \frac{1}{0.05(j\omega)^2 + 0.001(j\omega) + 1} \\ &= \frac{1}{1 - 0.05\omega^2 + j0.001\omega} \end{aligned}$$


BLOCK DIAGRAM REDUCTION

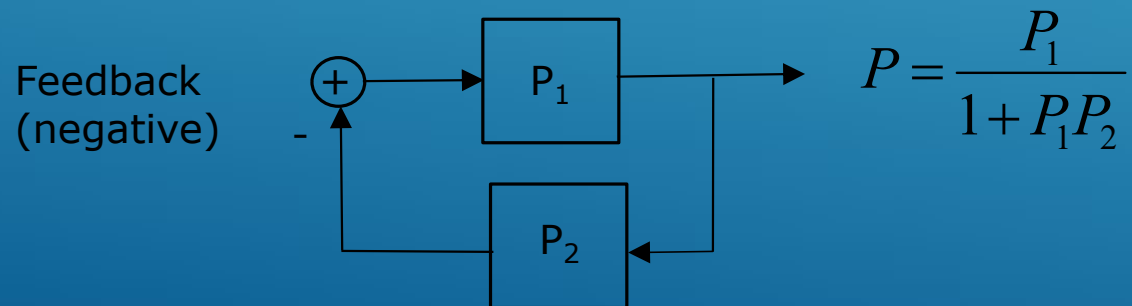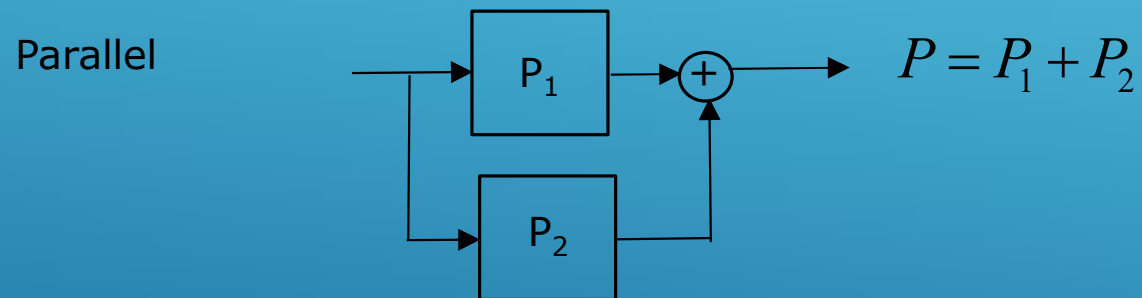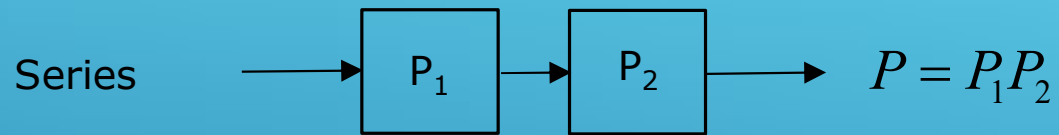


EX. PASSIVE LOW-PASS FILTER (LPF)

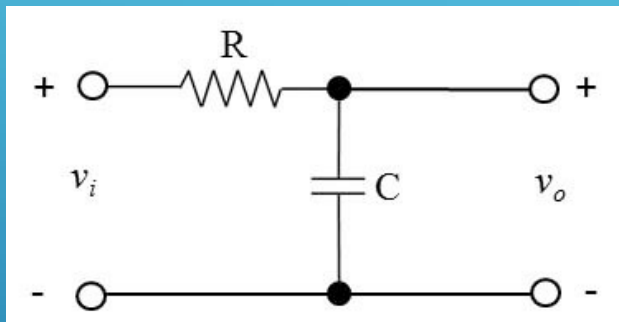


$$\omega_o = 2\pi f = \frac{1}{RC}$$

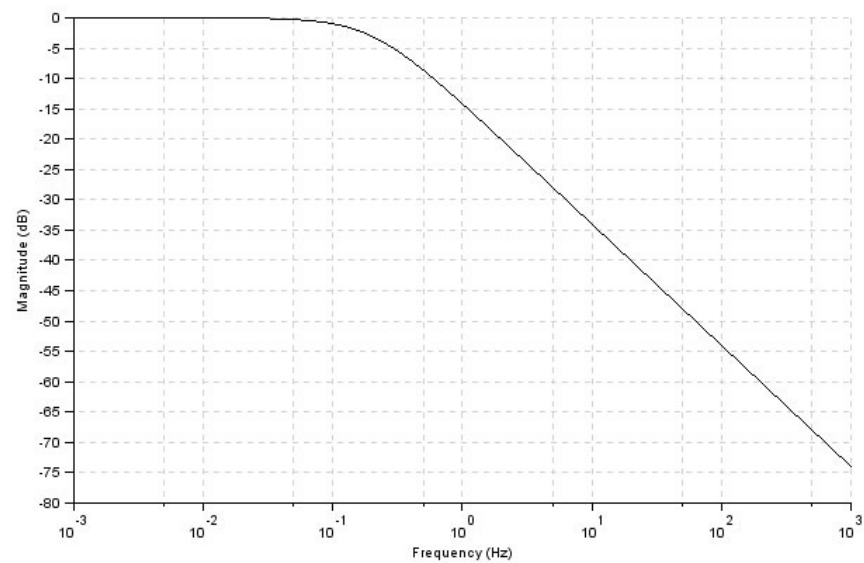


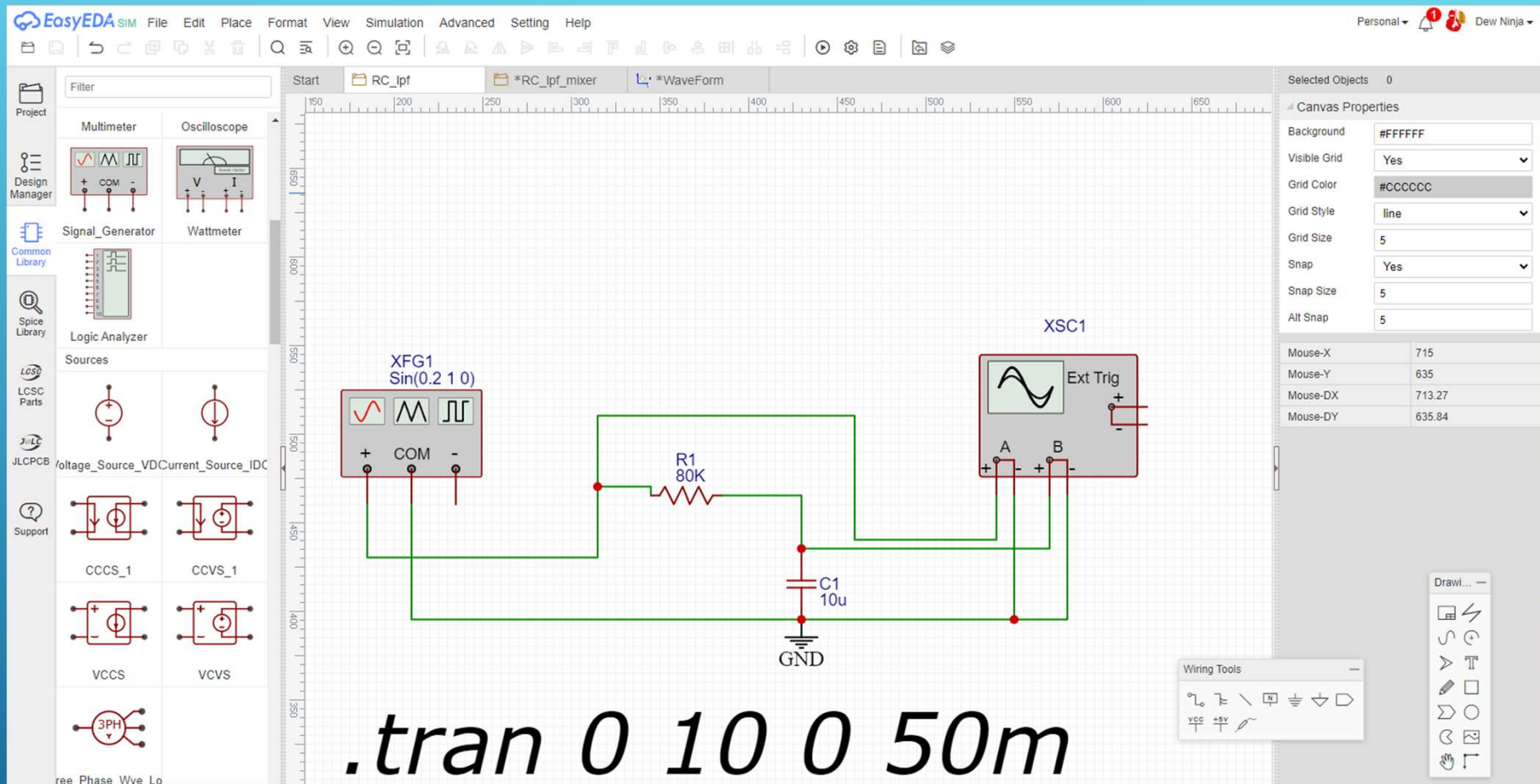


LPF SIMULATION ON EASYEDA

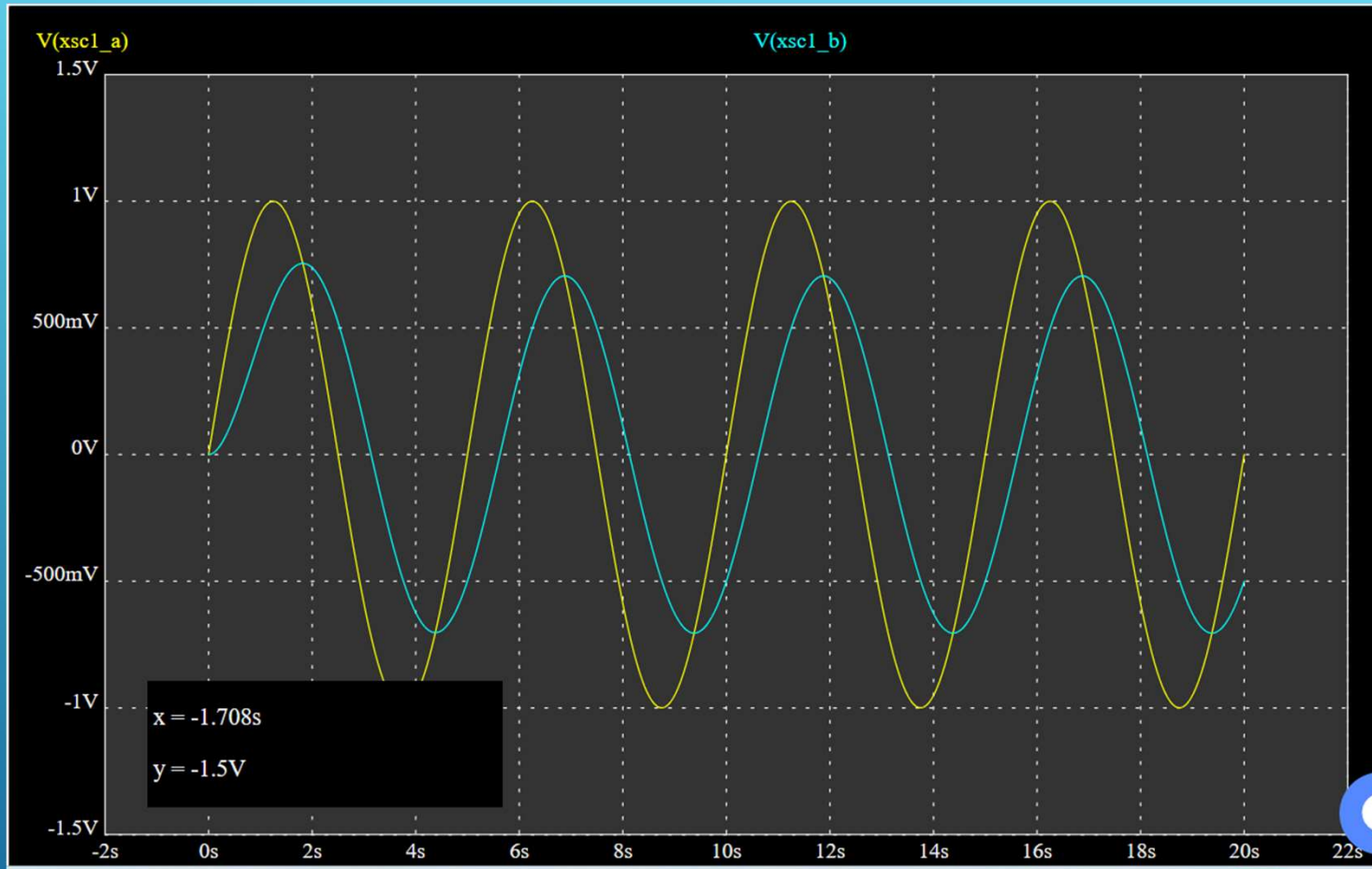

INPUT-OUTPUT FROM OSCILLOSCOPE

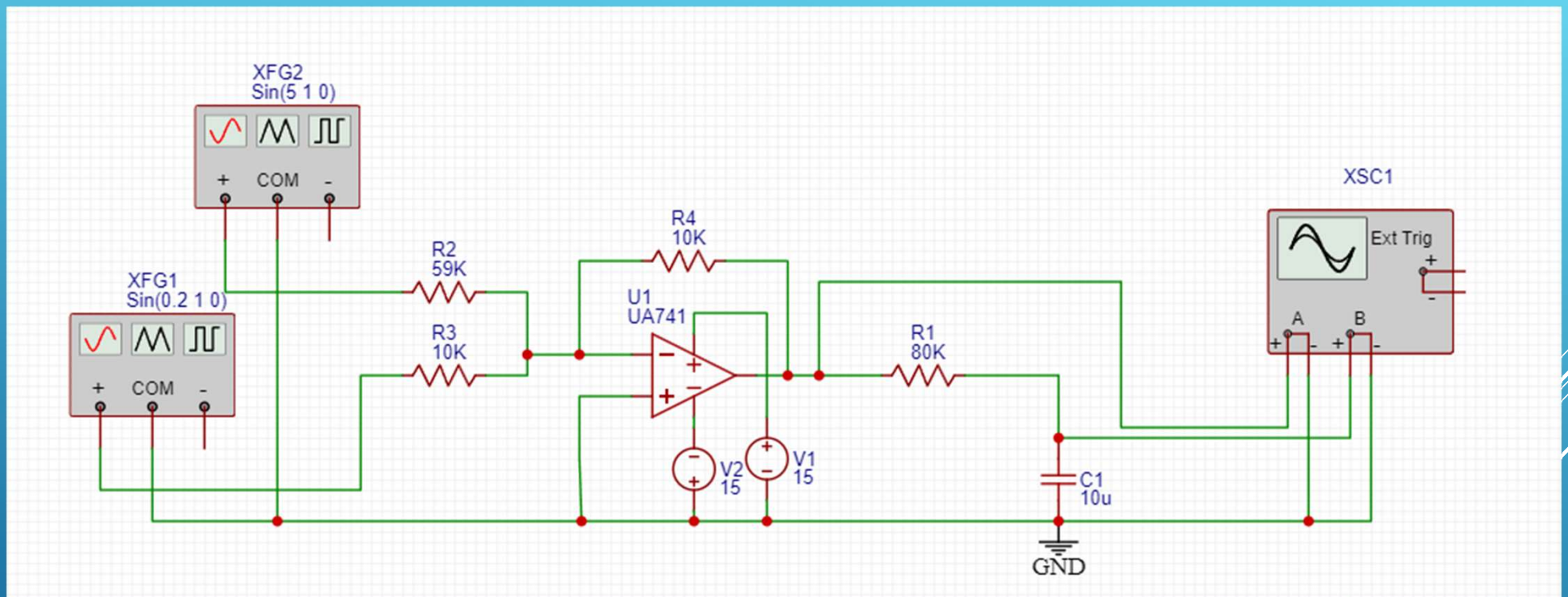


SIGNAL + NOISE SIMULATION

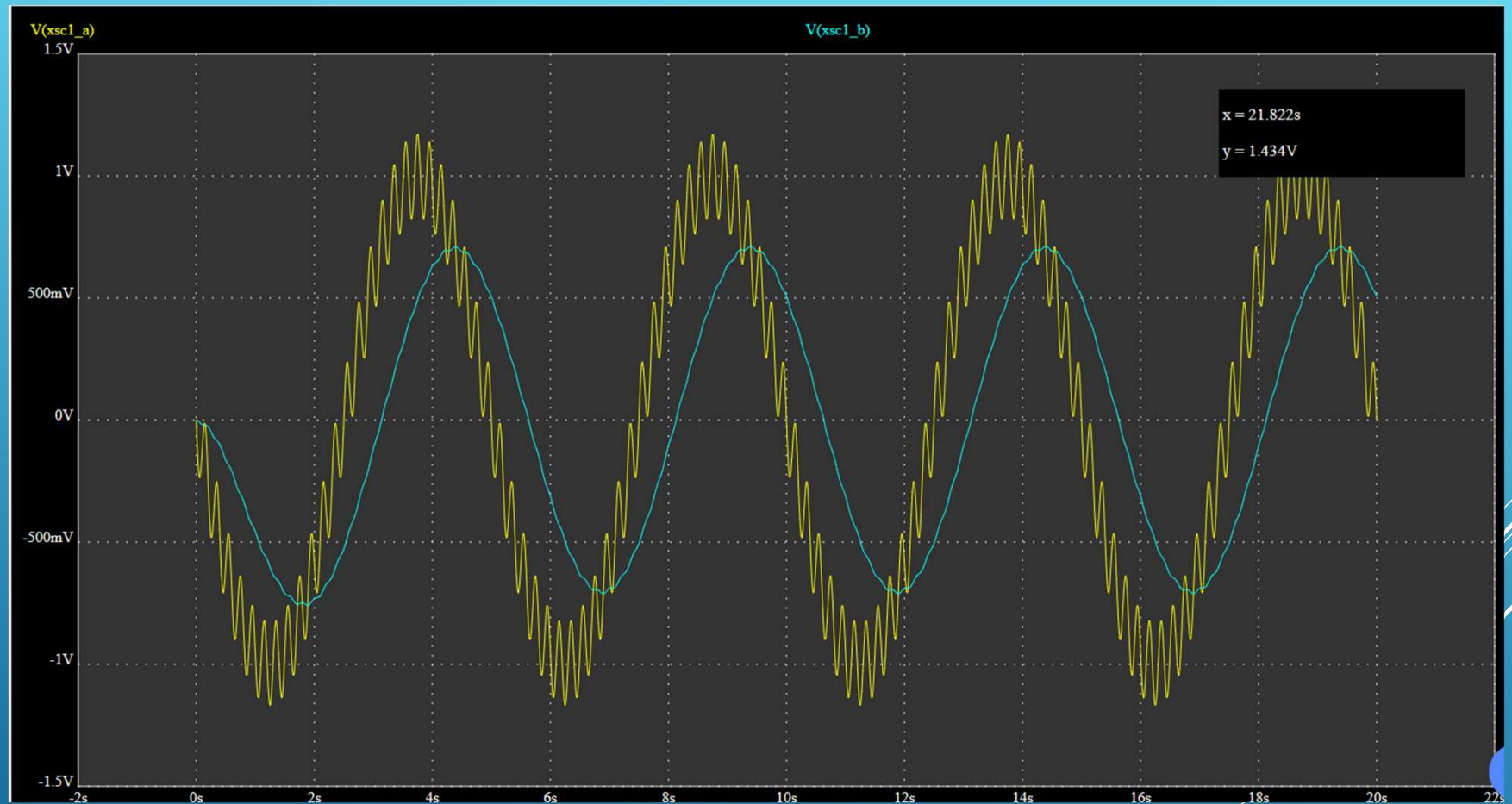

INPUT – OUTPUT COMPARISION

EXERCISE:

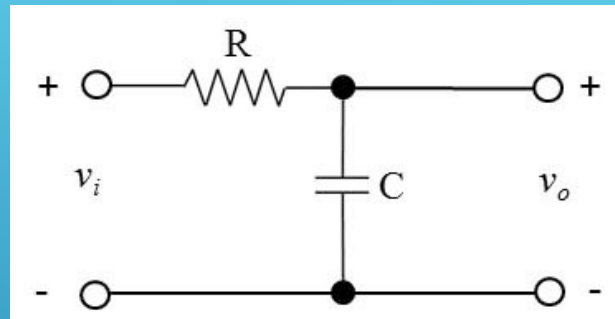

- ▶ Design an LPF filter with cutoff frequency 5 Hz
- ▶ Plot frequency response
- ▶ Apply base frequency (1 Hz) plus noise (20 Hz) to the LPF. Compare input and output signals

OTHER NOISE FILTERING METHODS

- ▶ Moving average
- ▶ Exponentially-weighted moving average

see `averaging.ipynb`

