


Lecture 1 : Basic circuit analysis and simulation

01205479 IoT for EE

Dr.Varodom Toochinda

Dept. of Mechanical Engineering, Kasetsart University


Resistance

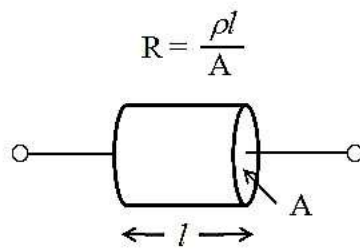


Physical



symbol

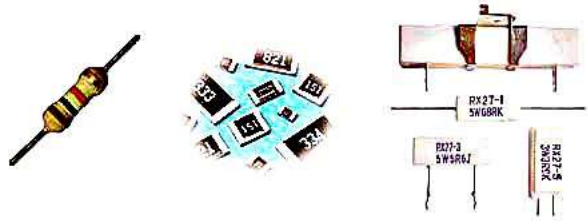

Resistors

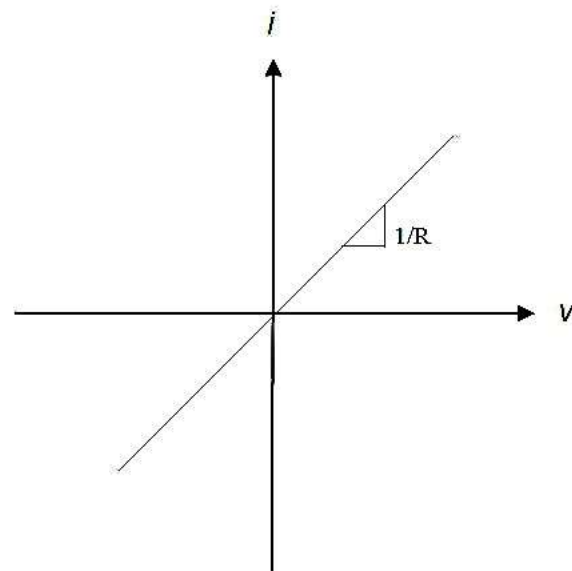

i-v characteristics

Basic Relationships

- Ohm's Law

$$V = IR$$

- Power

$$P = VI = \frac{V^2}{R} = I^2 R$$

Kirchhoff's Current and Voltage Laws

- KCL



$$\sum_{n=1}^N i_n = 0$$

- KVL


$$\sum_{n=1}^N v_n = 0$$

KCL and KVL applications

- ▶ Total resistance
 - ▶ Series
 - ▶ Parallel
- ▶ Current and voltage divider

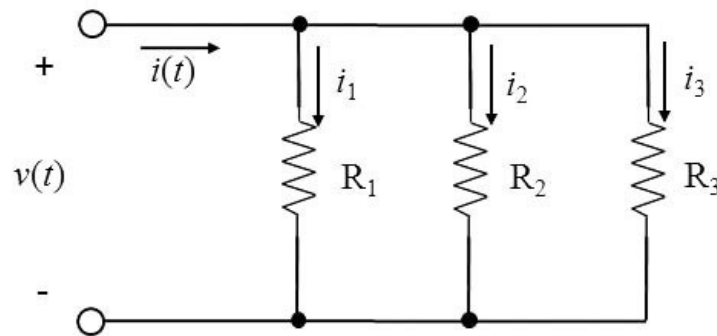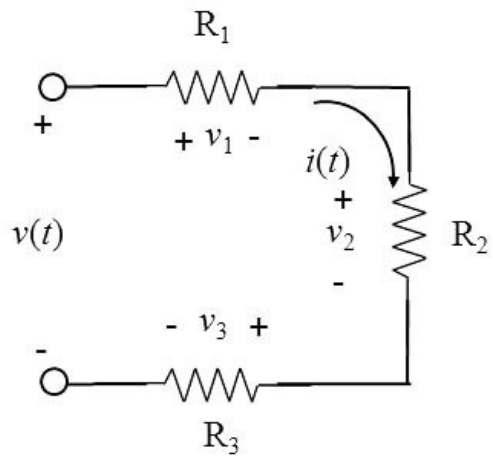


Exercise1 : Wheatstone bridge

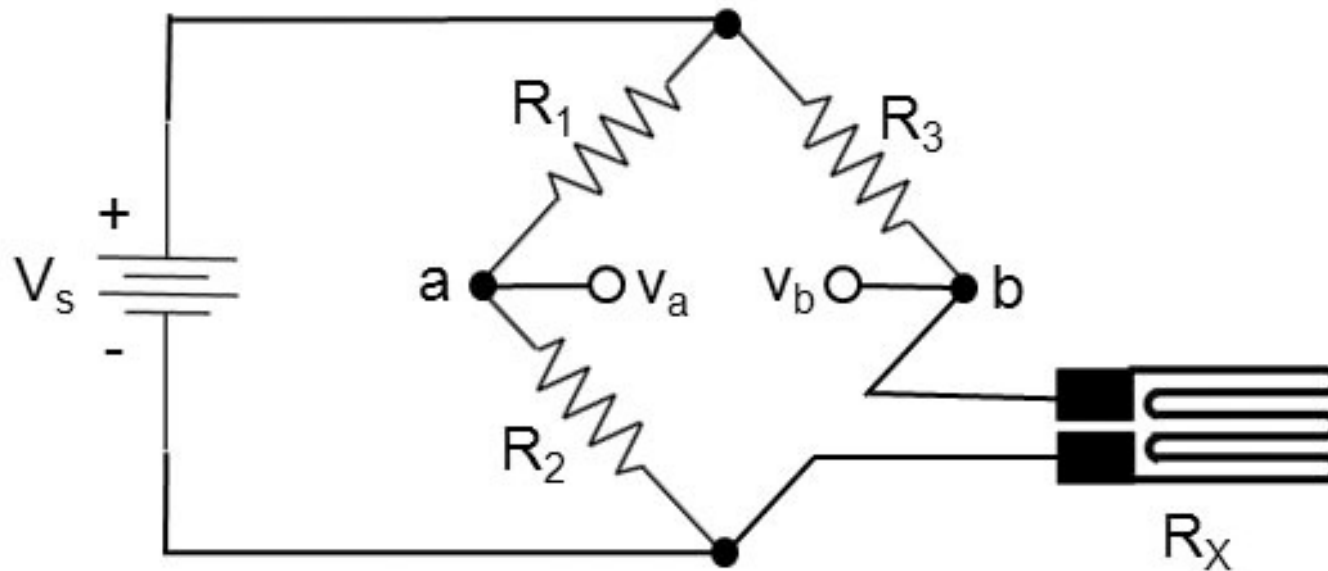

Let $V_s = 5$ Volts. $R_1 = R_2 = R_3 = 1000$ Ohms, R_x varies between $800 - 1200$ Ohms
Compute the corresponding voltage range for V_{ab} .

Simulate on EasyEDA

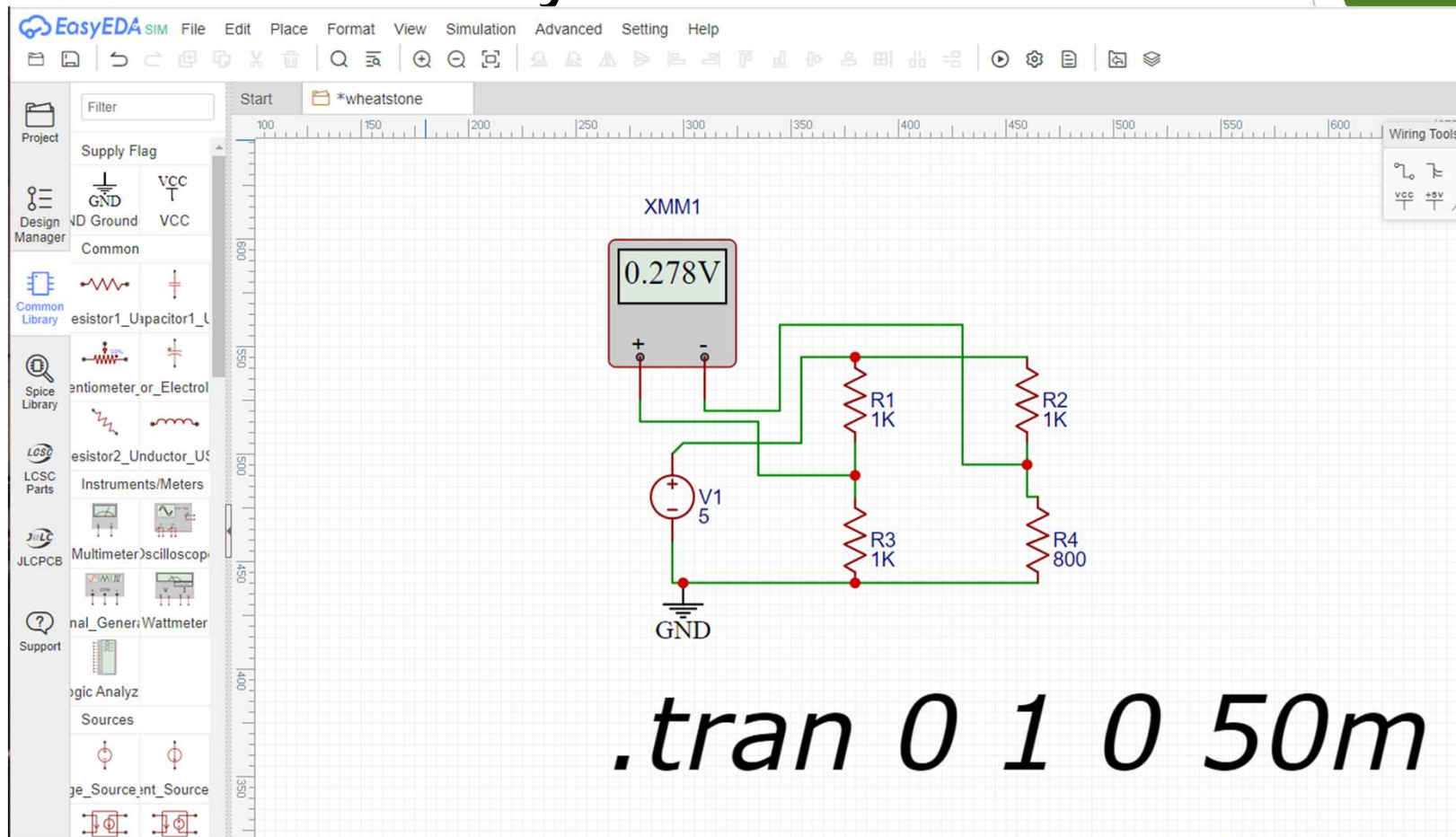


Circuit analysis methods

- ▶ Node voltage
- ▶ Mesh current
- ▶ Superposition
- ▶ Equivalent circuit/source transformation
 - ▶ Thevenin voltage source
 - ▶ Norton current source




Node voltage analysis

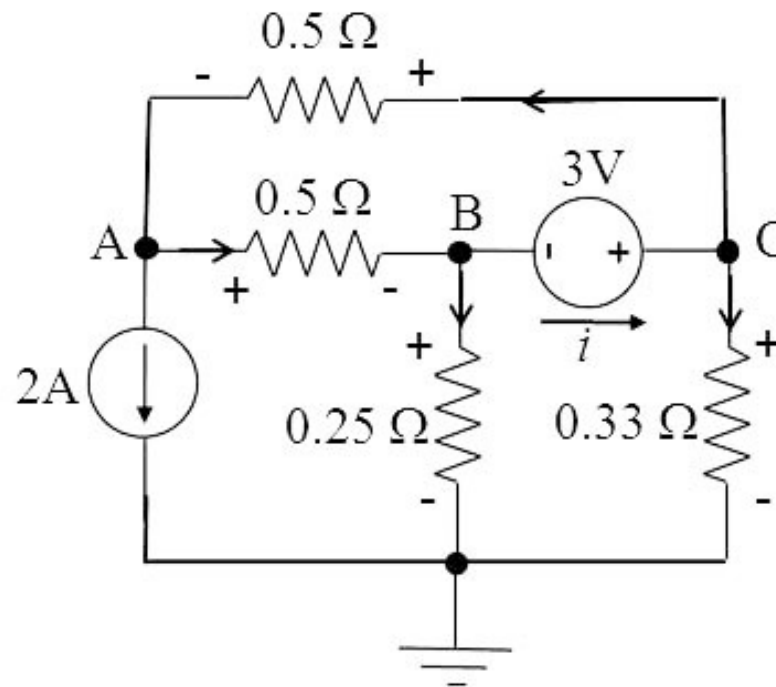- Assign V_A , V_B , V_C as variables
- Use KCL to solve




Mesh current analysis

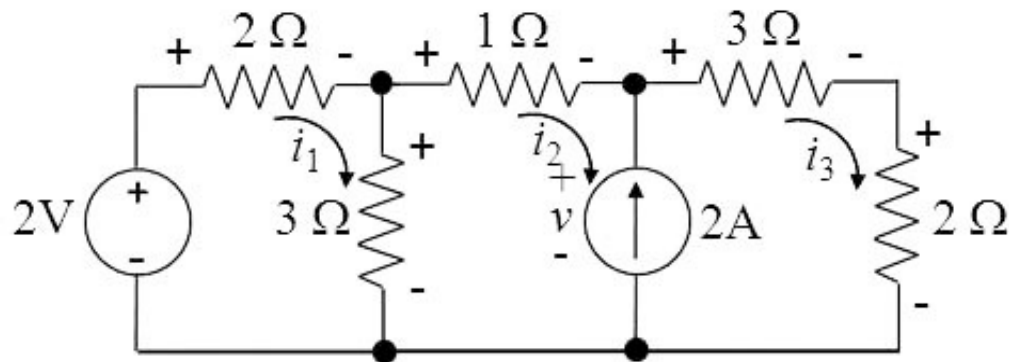- Assign i_1 , i_2 , i_3 as variables
- Use KVL to solve





Superposition method

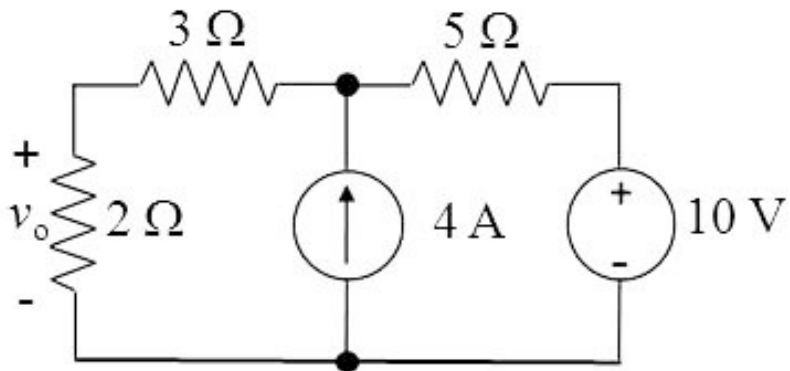

$$V_{o1} = (2 / (2 + 3 + 5)) * 10 = 2 \text{ V}$$


$$V_{o2} = 2 * 2 = 4 \text{ V}$$

$$V_o = 2 + 4 = 6 \text{ V}$$

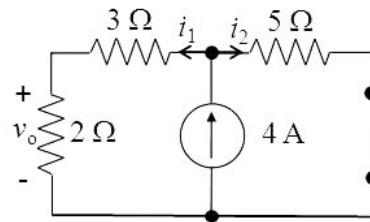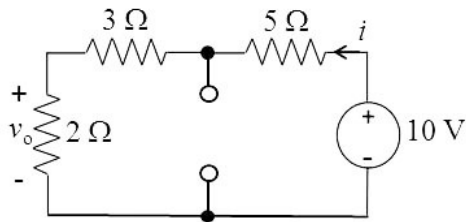


Exercise : simulate on EasyEDA


Equivalent circuit concept

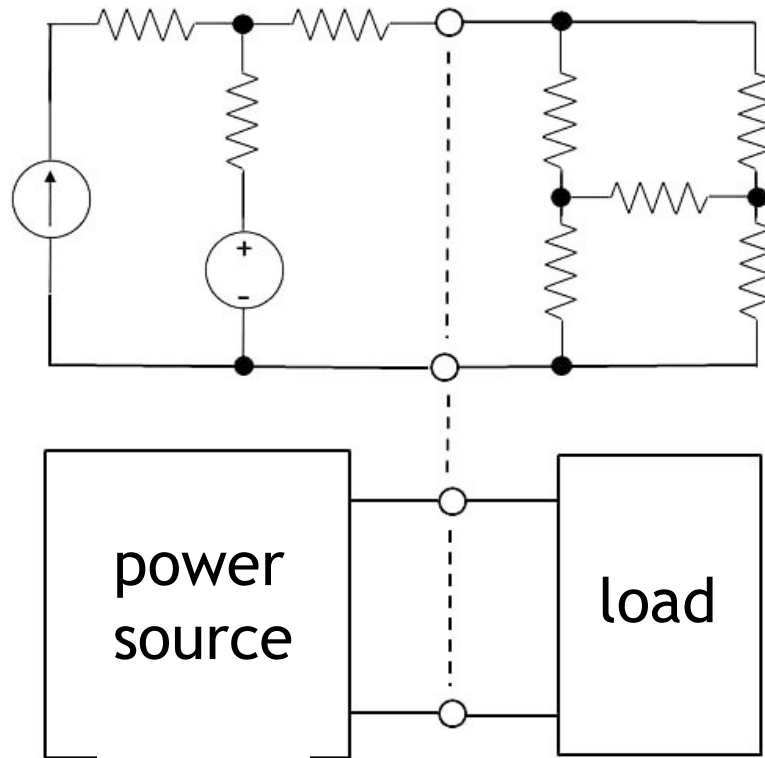


Thevenin source

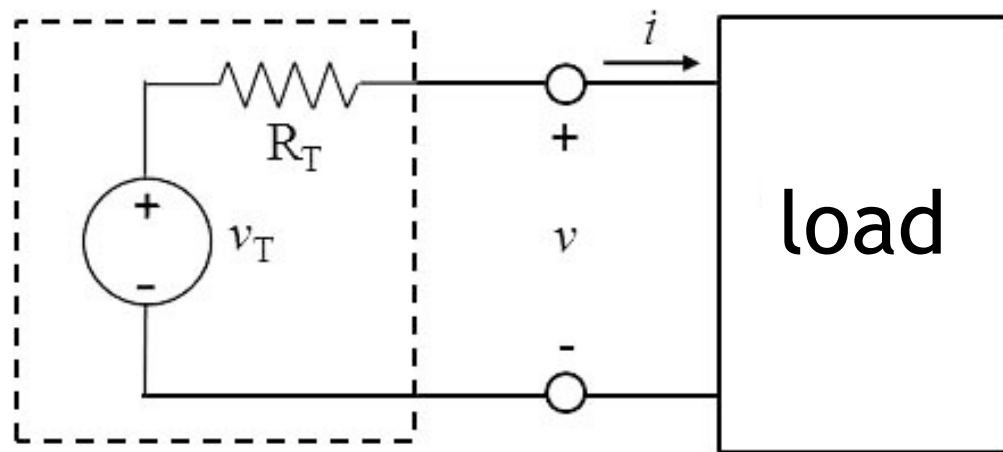


Norton source

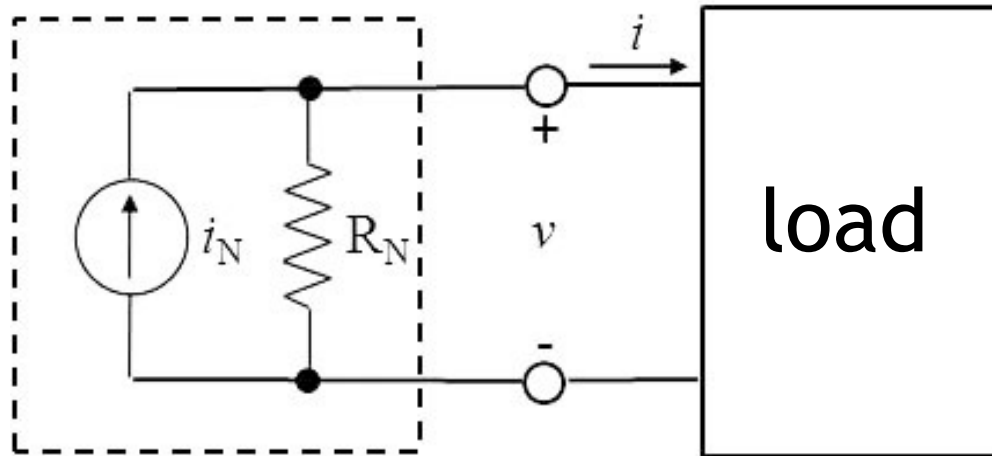


Example : Thevenin equivalent source

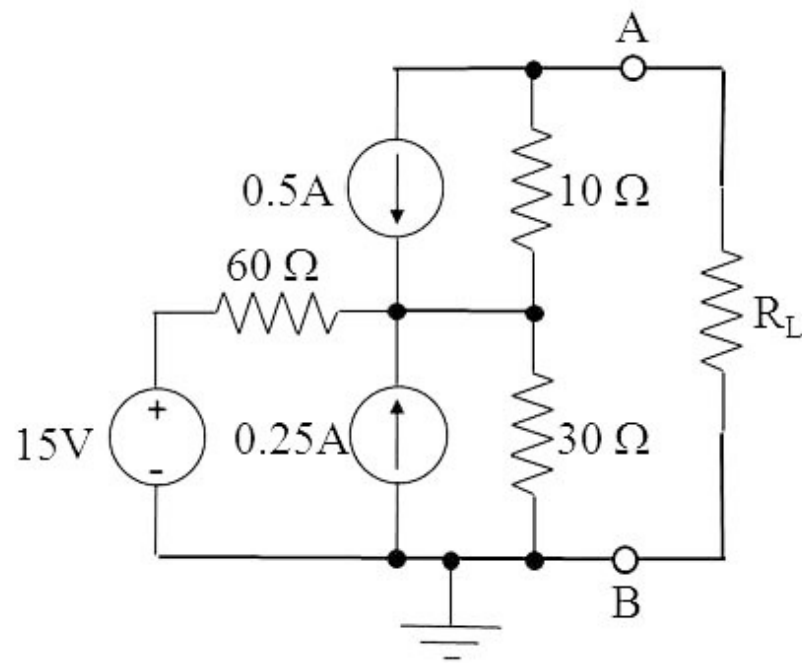


Compute Thevenin resistance

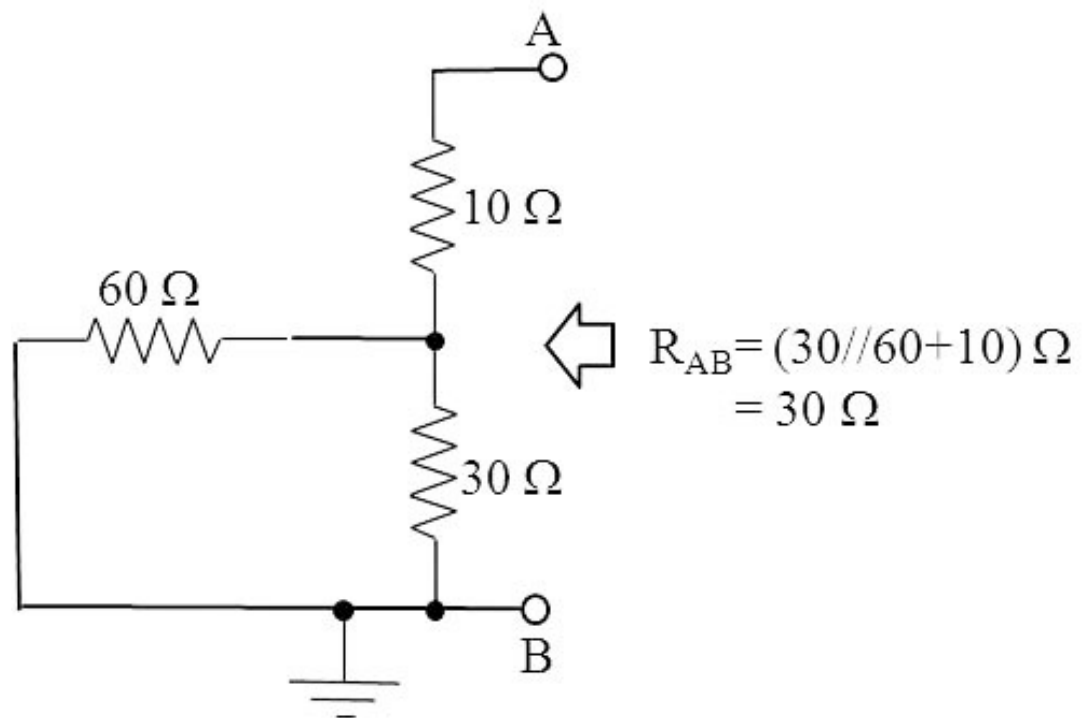

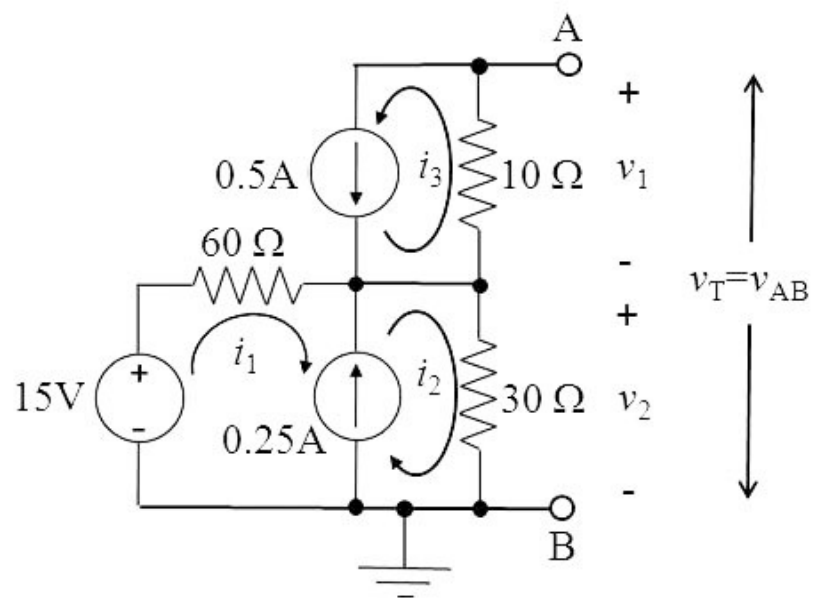




Compute
Thevenin
voltage

Thevenin equivalent circuit

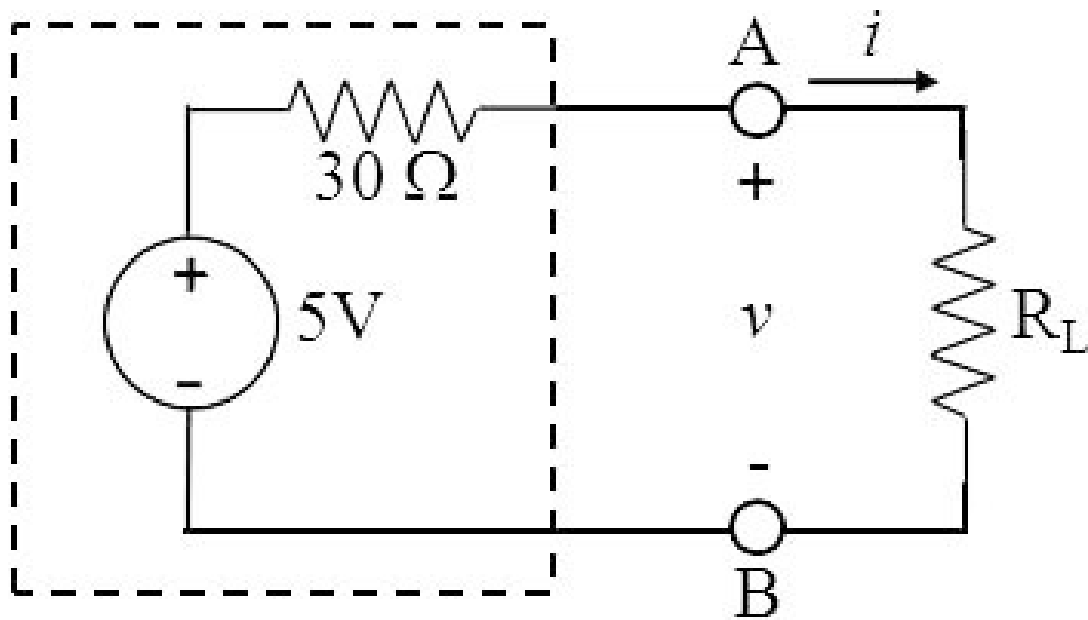

Source transformation

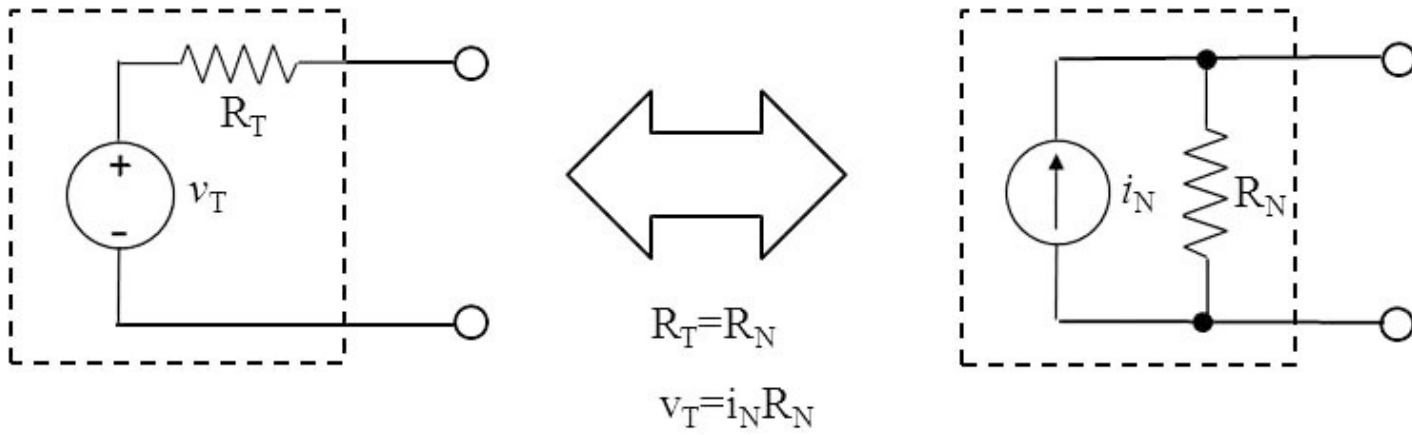


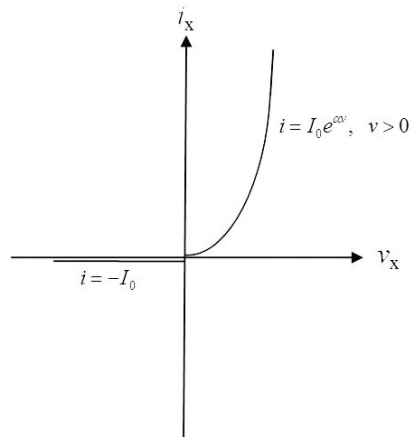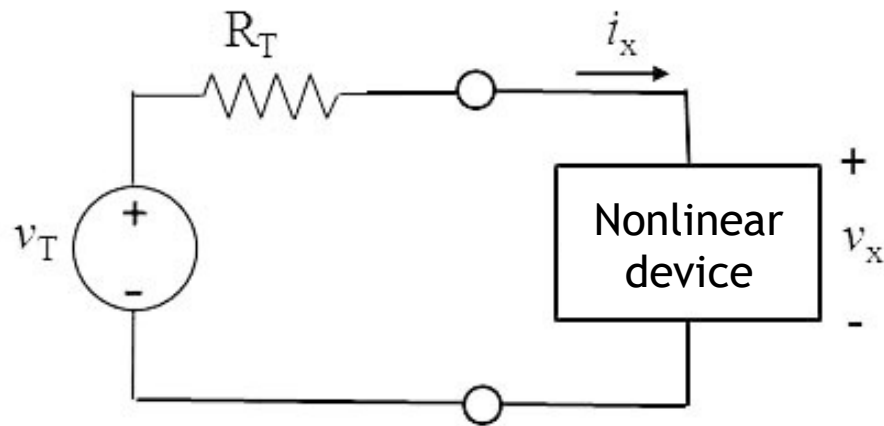

Nonlinear load


- Load-line analysis
- Numerical method

Load-line analysis

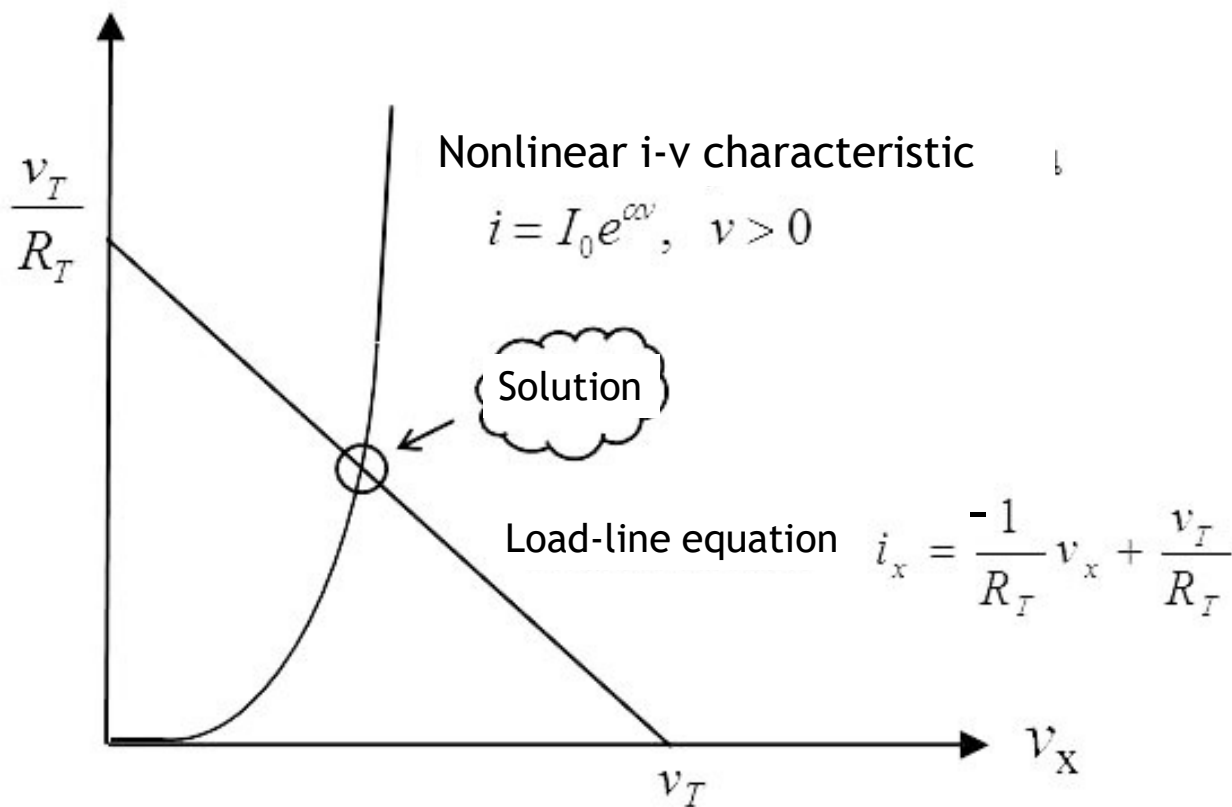

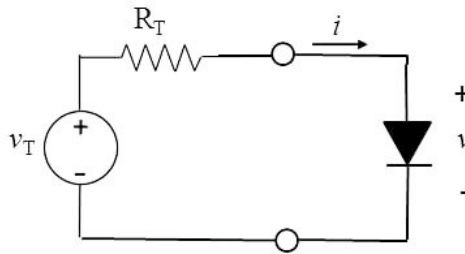Exercise 2: Find current and voltage at diode by load-line and numerical methods

$$R_T = 22\Omega, \quad V_T = 12\text{ V}$$




Diode i-v characteristic

$$i_D = I_{SAT} \left(\exp \left\{ \frac{v_D}{kT/q} \right\} - 1 \right)$$

at room temperature

$$I_{SAT} = 10^{-12} \text{ A}$$

$$\frac{kT}{q} = 0.0259 \text{ V}$$

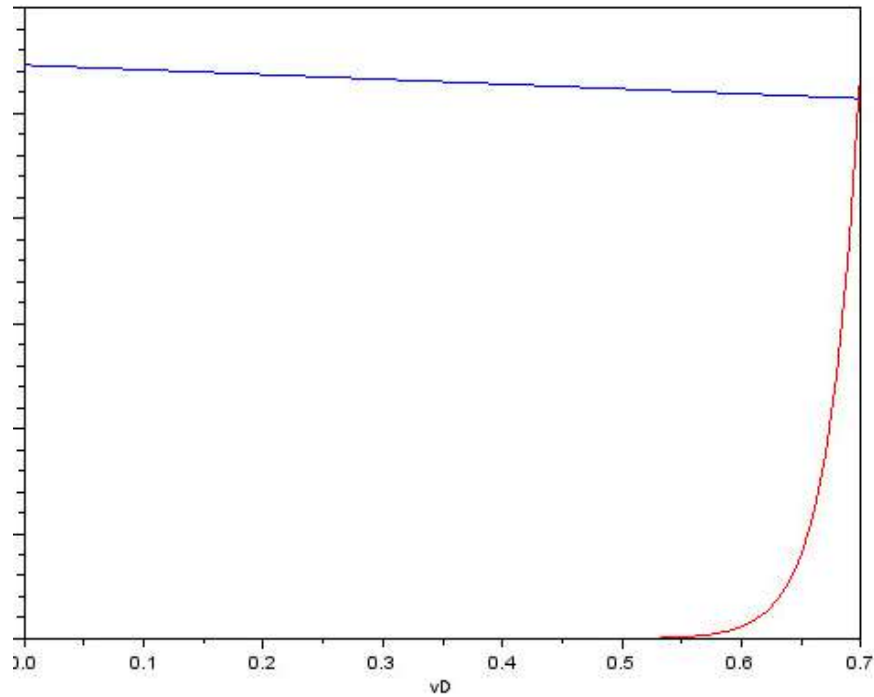

Load-line
analysis
using Scilab
plot

Flowchart of numerical method

